
Chapter 5, Solution 6.

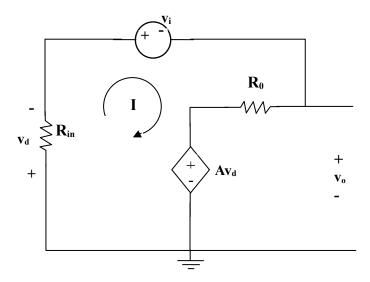

$$(R_0 + R_i)R + v_i + Av_d = 0$$

But $v_d = R_i I$,

$$v_i + (R_0 + R_i + R_i A)I = 0$$

$$I = \frac{-v_i}{R_0 + (1+A)R_i}$$
 (1)

$$-Av_d - R_0I + v_o = 0$$

 $v_o = Av_d + R_0I = (R_0 + R_iA)I$ Substituting for I in (1),

$$\begin{aligned} \mathbf{v}_0 &= -\left(\frac{\mathbf{R}_0 + \mathbf{R}_i \mathbf{A}}{\mathbf{R}_0 + (1+\mathbf{A})\mathbf{R}_i}\right) \mathbf{v}_i \\ &= -\frac{\left(50 + 2x10^6 \, x2x10^5\right) \cdot 10^{-3}}{50 + \left(1 + 2x10^5\right) x2x10^6} \\ &\cong \frac{-200,000 \, x2x10^6}{200,001 \, x2x10^6} \, \text{mV} \end{aligned}$$

$$v_0 = -0.999995 \text{ mV}$$