

Chapter 5, Problem 77

Solve Prob. 5.48 using *PSpice* and op amp LM324.

5,48 The circuit in Fig. 5.78 is a differential amplifier driven by a bridge. Find v_o .

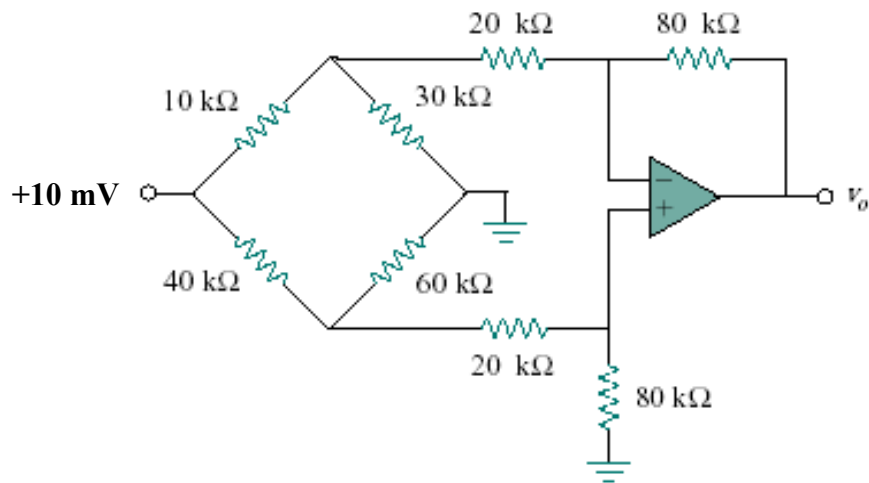


Figure 5.78
For Prob. 5.48 and 5.77.