

Chapter 10, Solution 45.

Use superposition to find $i(t)$ in the circuit of Fig. 10.90.


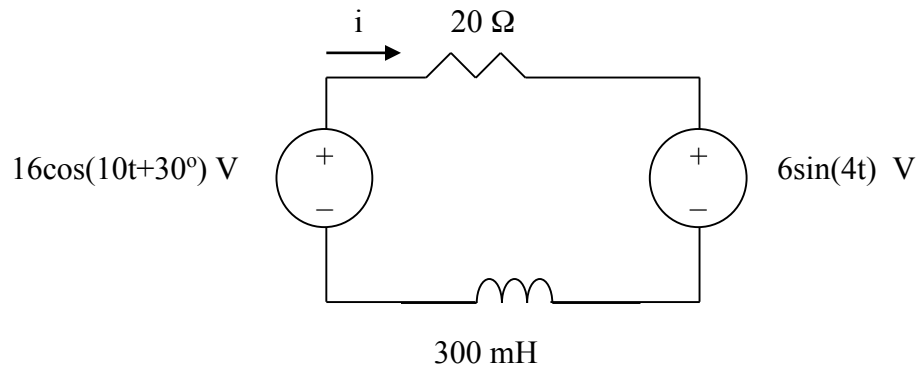


Figure 10.90
For Prob. 10.45.

Solution

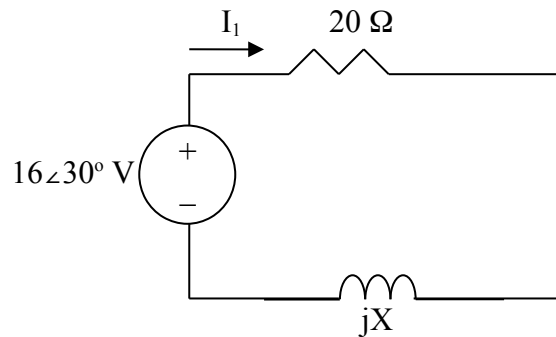Let $i = i_1 + i_2$, where i_1 and i_2 are due to $16\cos(10t + 30^\circ)$ and $6\sin 4t$ sources respectively. To find i_1 , consider the circuit below.




$$X = \omega L = 10 \times 300 \times 10^{-3} = 3$$

Type equation here.

$$I_1 = \frac{16 \angle 30^\circ}{20 + j3} = \frac{16 \angle 30^\circ}{20.22 \angle 8.53^\circ} = 0.7913 \angle 21.47^\circ$$

$$i_1(t) = 791.1 \cos(10t + 21.47^\circ) \text{ mA.}$$

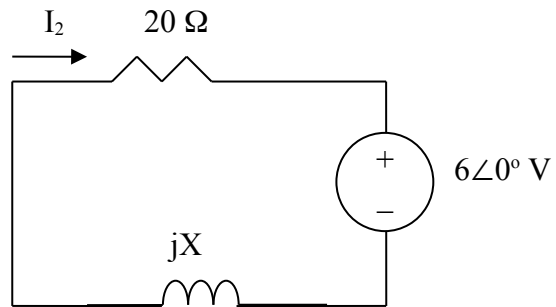To find $i_2(t)$, consider the circuit below,



$$X = \omega L = 4 \times 300 \times 10^{-3} = 1.2$$

$$I_2 = \frac{-6 \angle 0^\circ}{20 + j1.2} = \frac{6 \angle 180^\circ}{20.036 \angle 3.43^\circ} = 0.2995 \angle 176.57^\circ \text{ or}$$

$$i_2(t) = 299.5 \sin(4t + 176.57^\circ) \text{ mA.}$$

Thus,

$$i(t) = i_1(t) + i_2(t) = [791.1 \cos(10t + 21.47^\circ) + 299.5 \sin(4t + 176.57^\circ)] \text{ mA.}$$