

Chapter 7, Problem 55.

Find $v(t)$ for $t < 0$ and $t > 0$ in the circuit in Fig. 7.121.

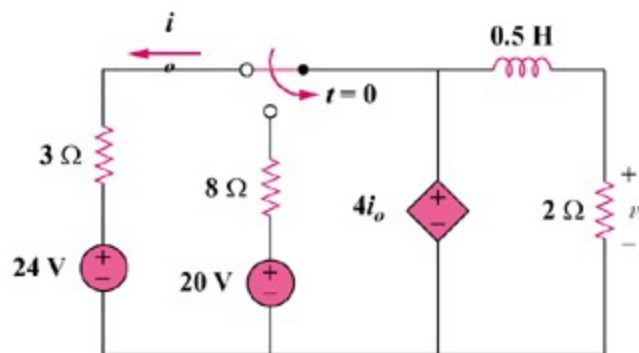


Figure 7.121
For Prob. 7.55.