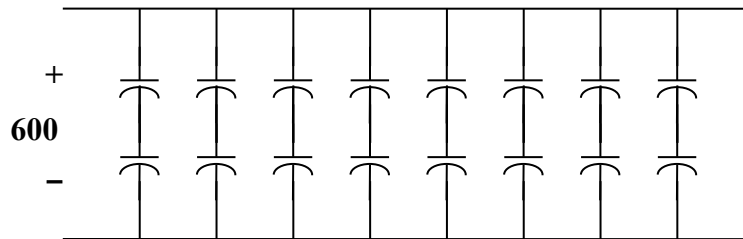


### Chapter 6, Solution 83.

Your laboratory has available a large number of  $10\text{-}\mu\text{F}$  capacitors rated at  $300\text{ V}$ . To design a capacitor bank of  $40\text{-}\mu\text{F}$  rated at  $600\text{ V}$ , how many  $10\text{-}\mu\text{F}$  capacitors are needed and how would you connect them?

#### Solution

Since two  $10\mu\text{F}$  capacitors in series gives  $5\mu\text{F}$ , rated at  $600\text{V}$ , it requires 8 groups in parallel with each group consisting of two capacitors in series, as shown below:



Answer: **Eight groups in parallel with each group made up of two capacitors in series.**