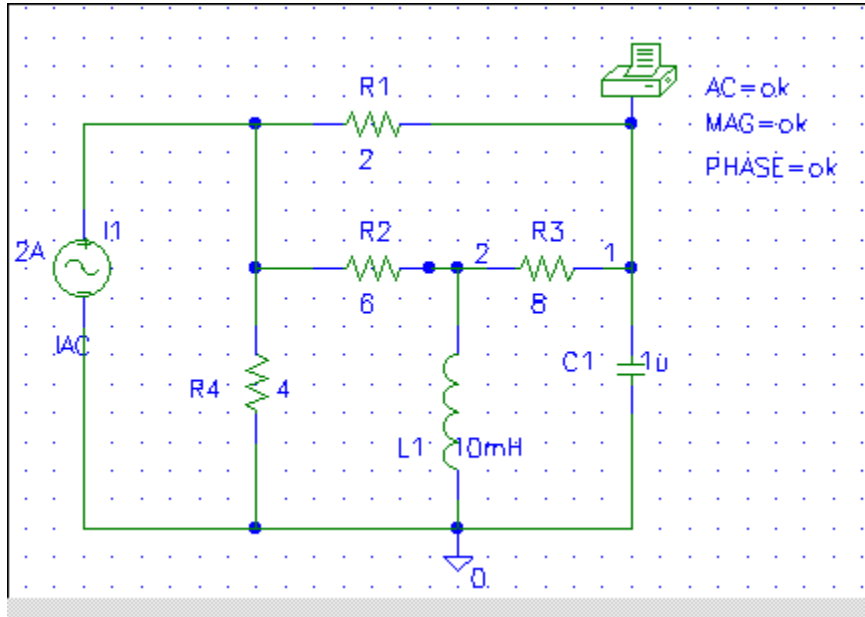


### Chapter 10, Solution 83.

The schematic is shown below. The frequency is  $f = \omega / 2\pi = \frac{1000}{2\pi} = 159.15$



When the circuit is saved and simulated, we obtain from the output file

FREQ	VM(1)	VP(1)
1.592E+02	6.611E+00	-1.592E+02

Thus,

$$v_o = 6.611 \cos(1000t - 159.2^\circ) \text{ V}$$