

Chapter 11, Problem 89.

An industrial heater has a nameplate which reads:

210 V 60 Hz 12 kVA 0.78 pf lagging

Determine:

- (a) the apparent and the complex power
- (b) the impedance of the heater