

### Chapter 5, Problem 20

In the circuit in Fig. 5.59, calculate  $v_o$  if  $v_s = 2$  V.

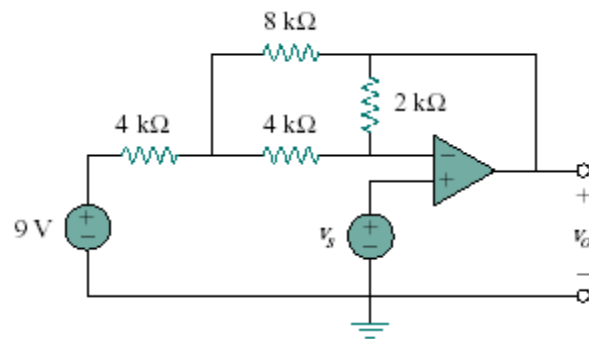


Figure 5.59  
For Prob. 5.20.