

Chapter 5, Problem 3

Determine the output voltage when $20\ \mu\text{V}$ is applied to the inverting terminal of an op amp and $+30\ \mu\text{V}$ to its noninverting terminal. Assume that the op amp has an open-loop gain of 200,000.