

**Chapter 10, Problem 19.**

Obtain  $V_o$  in Fig. 10.68 using nodal analysis.

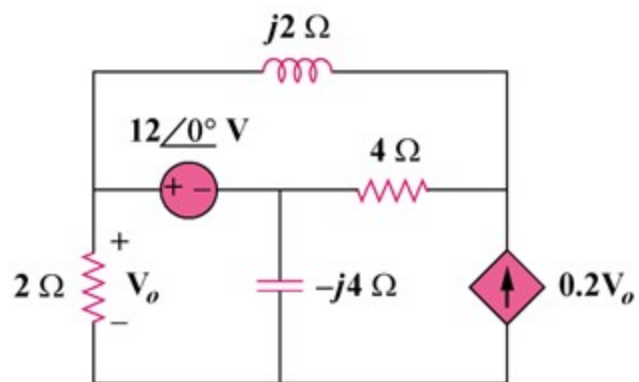


Figure 10.68  
For Prob. 10.19.