

### Chapter 11, Solution 16.

For the circuit in Fig. 11.47, find the maximum power that can be delivered to the load  $\mathbf{Z}_L$ .


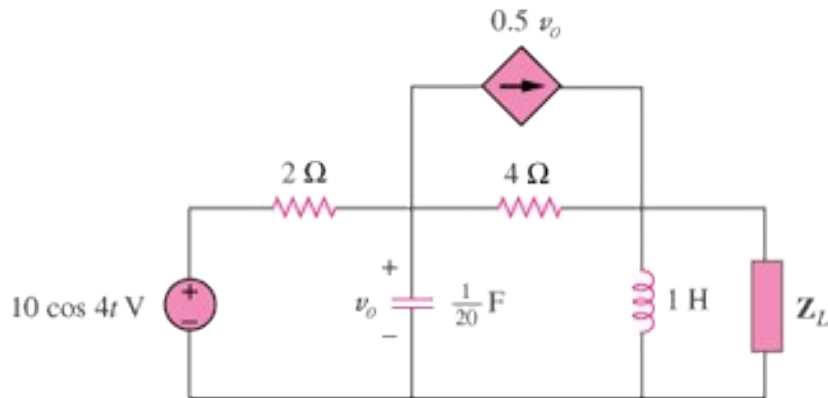


Figure 11.47  
For Prob. 11.16.
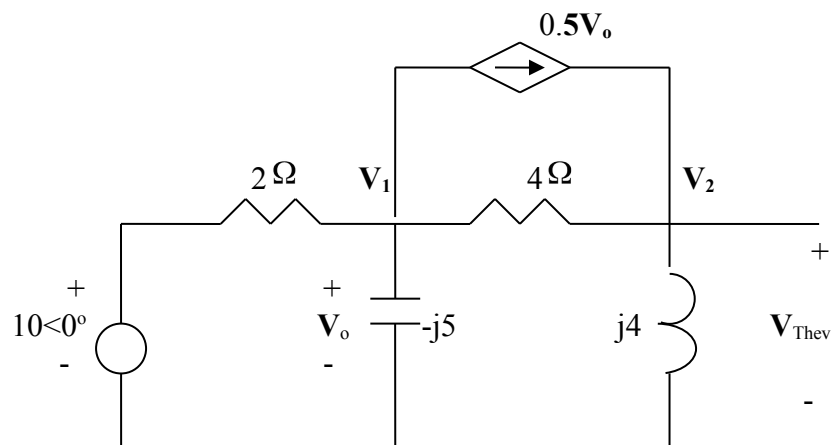
### Solution

$$\omega = 4, \quad 1\text{ H} \longrightarrow j\omega L = j4, \quad 1/20\text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j4 \times 1/20} = -j5$$

We find the Thevenin equivalent at the terminals of  $\mathbf{Z}_L$ . To find  $\mathbf{V}_{\text{Thev}}$ , we use the circuit shown below.



At node 1,

$$\frac{10 - V_1}{2} = \frac{V_1}{-j5} + 0.5V_1 + \frac{V_1 - V_2}{4} \longrightarrow 5 = V_1(1.25 + j0.2) - 0.25V_2 \quad (1)$$


At node 2,

$$\frac{V_1 - V_2}{4} + 0.25V_1 = \frac{V_2}{j4} \longrightarrow 0 = 0.5V_1 + V_2(-0.25 + j0.25) \quad (2)$$

Solving (1) and (2) leads to

$$V_{Thev} = V_2 = 6.1947 + j7.0796 = 9.4072 \angle 48.81^\circ$$

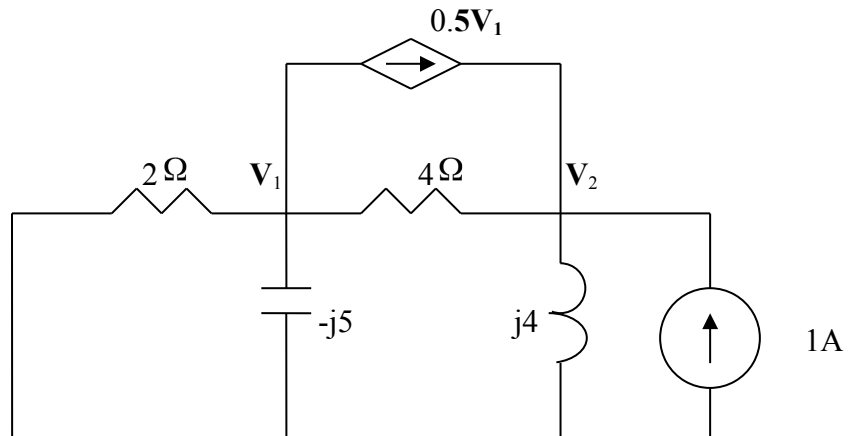To obtain  $R_{eq}$ , consider the circuit shown below. We replace  $Z_L$  by a 1-A current source.



At node 1,

$$\frac{V_1}{2} + \frac{V_1}{-j5} + 0.25V_1 + \frac{V_1 - V_2}{4} = 0 \longrightarrow 0 = V_1(1 + j0.2) - 0.25V_2 \quad (3)$$

At node 2,

$$1 + \frac{V_1 - V_2}{4} + 0.25V_1 = \frac{V_2}{j4} \longrightarrow -1 = 0.5V_1 + V_2(-0.25 + j0.25) \quad (4)$$

Solving (1) and (2) gives

$$Z_{eq} = \frac{V_2}{1} = 1.9115 + j3.3274 = 3.837 \angle 60.12^\circ \quad \text{and } Z_L = 3.837 \angle -60.12^\circ \Omega$$

$$P_{\max} = \frac{|V_{Th}|^2}{2|Z_{eq} - Z_L|^2} 1.9115 = \frac{9.4072^2}{2 \times 4 \times 1.9115} = 5.787 \text{ W}$$