

**Chapter 6, Problem 39.**

The voltage across a 200-mH inductor is given by

$$v(t) = [3t^2 + 2t + 4] \text{ V for } t > 0.$$

Determine the current  $i(t)$  through the inductor. Assume that  $i(0) = 1 \text{ A}$ .