

**Chapter 6, Problem 56.**

Find  $L_{eq}$  in the circuit in Fig. 6.78.

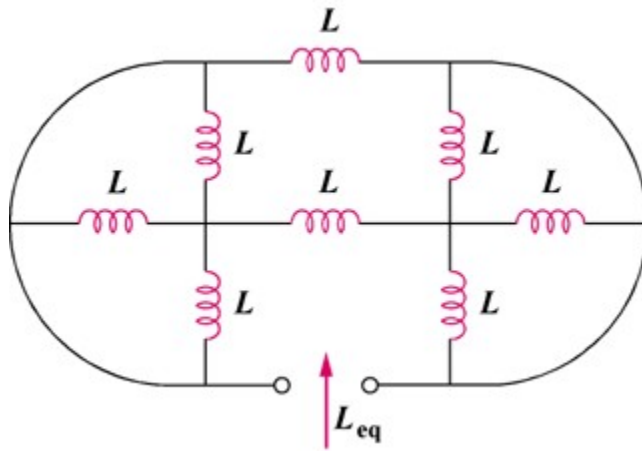


Figure 6.78  
For Prob. 6.56.