

Chapter 11, Problem 18.

Find the value of \mathbf{Z}_L in the circuit of Fig. 11.49 for maximum power transfer.

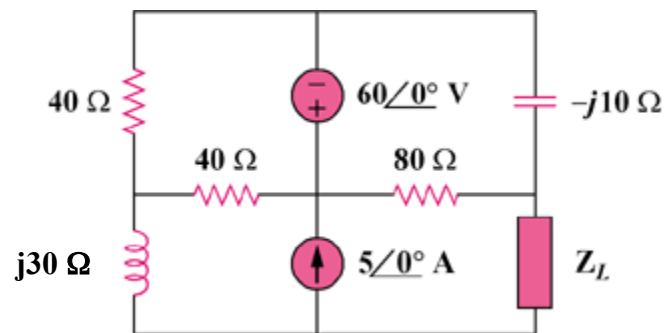


Figure 11.49
For Prob. 11.18.