
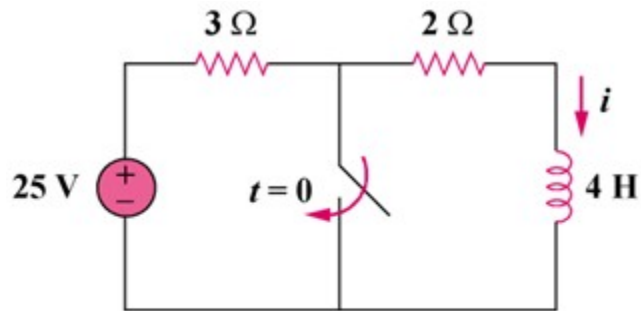


Chapter 7, Problem 53.

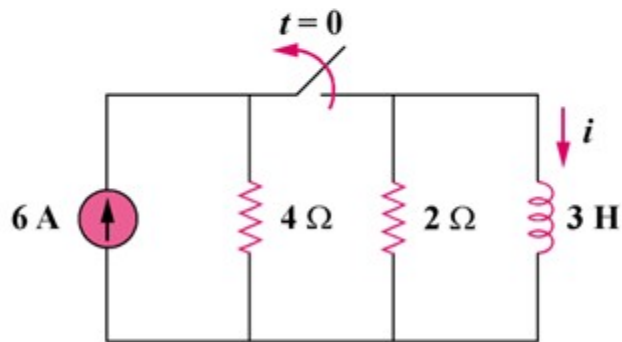Determine the inductor current $i(t)$ for both $t < 0$ and $t > 0$ for each of the circuits in Fig. 7.119.



(a)



(b)

Figure 7.119
For Prob. 7.53.