

**Chapter 6, Problem 73.**

Show that the circuit in Fig. 6.90 is a noninverting integrator.

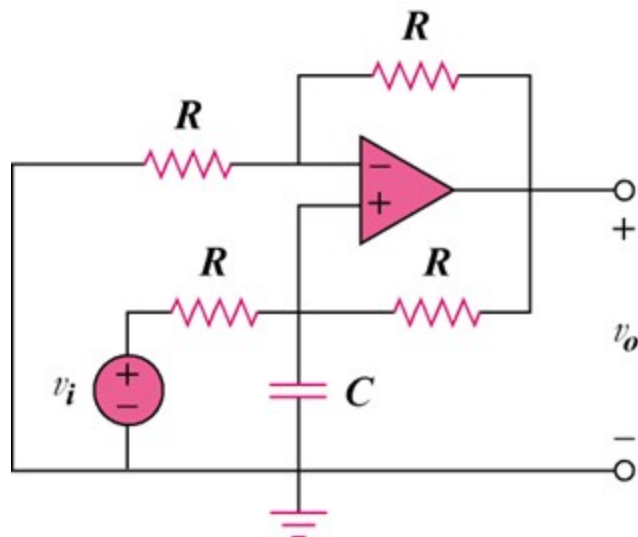


Figure 6.90  
For Prob. 6.73.