

Chapter 9, Solution 29.

Given that $v_C(0) = 2\cos(155^\circ)$ V, what is the instantaneous voltage across a $2\text{-}\mu\text{F}$ capacitor when the current through it is $i = 4 \sin(10^6 t + 25^\circ)$ A?

Solution

$$Z = \frac{1}{j\omega C} = \frac{1}{j(10^6)(2 \times 10^{-6})} = -j 0.5$$

$$V = IZ = (4 \angle 25^\circ)(0.5 \angle -90^\circ) = 2 \angle -65^\circ$$

Therefore $v(t) = 2 \sin(10^6 t - 65^\circ)$ V.