

Chapter 10, Problem 92.

The oscillator circuit in Fig. 10.134 uses an ideal op amp.

- (a) Calculate the minimum value of R_o that will cause oscillation to occur,
- (b) Find the frequency of oscillation.

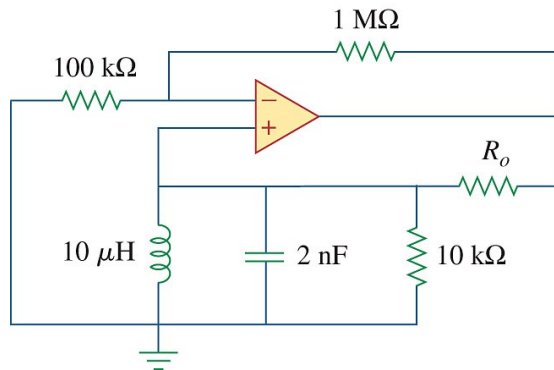


Figure 10.134
For Prob. 10.92.