

Chapter 10, Problem 10.

Use nodal analysis to find v_o in the circuit shown in Fig. 10.59. Let $\omega = 2 \text{ krad/s}$.

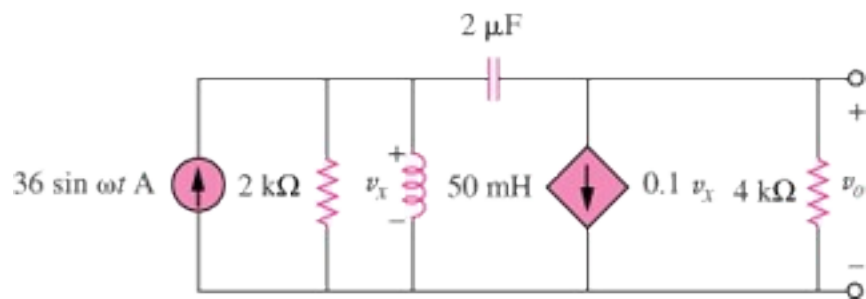


Figure 10.59
For Prob. 10.10.