

Chapter 7, Solution 75.

In the circuit of Fig. 7.140, find v_o and i_o , given that $v_s = 4 u(t)$ V and $v(0) = 1$ V.

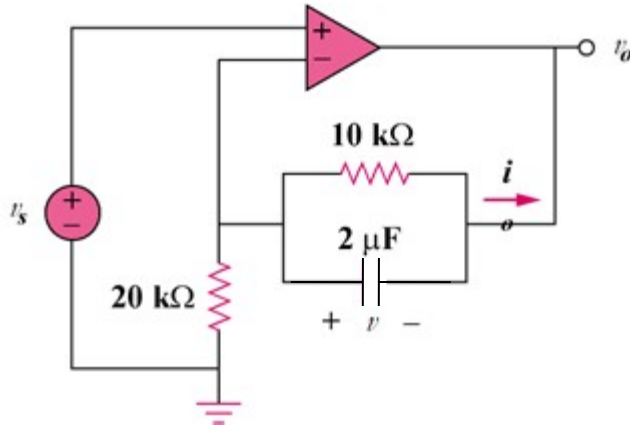


Figure 7.140
For Prob. 7.75.

Solution

Let v_1 = voltage at the noninverting terminal.

Let v_2 = voltage at the inverting terminal.

For $t > 0$, $v_1 = v_2 = v_s = 4$

$$\frac{0 - v_s}{R_1} = i_o, \quad R_1 = 20 \text{ k}\Omega$$

$$v_o = -i_o R$$

(1)

Also,
$$i_o = \frac{v}{R_2} + C \frac{dv}{dt}, \quad R_2 = 10 \text{ k}\Omega, \quad C = 2 \text{ }\mu\text{F}$$

i.e.
$$\frac{-v_s}{R_1} = \frac{v}{R_2} + C \frac{dv}{dt}$$

(2)

This is a step response.

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}, \quad v(0) = 1$$

where
$$\tau = R_2 C = (10 \times 10^3)(2 \times 10^{-6}) = \frac{1}{50}$$

At steady state, the capacitor acts like an open circuit so that i_o passes through R_2 . Hence, as $t \rightarrow \infty$

$$\frac{-V_s}{R_1} = i_o = \frac{v(\infty)}{R_2}$$

$$v(\infty) = \frac{-R_2}{R_1} V_s = \frac{-10}{20} (4) = -2$$

i.e.

$$v(t) = -2 + (1 + 2)e^{-50t}$$

$$v(t) = -2 + 3e^{-50t}$$

But $V = V_s - V_o$

or $V_o = V_s - v = 4 + 2 - 3e^{-50t}$

$$V_o = \mathbf{6 - 3e^{-50t} \text{ u(t)V}} = [6 - 3e^{-50t}]$$

$$i_o = \frac{-V_s}{R_1} = \frac{-4}{20k} = -0.2 \text{ mA}$$

or $i_o = \frac{v}{R_2} + C \frac{dv}{dt} = \mathbf{-0.2 \text{ mA}}$