

**Chapter 5, Problem 35**

Design a non-inverting amplifier with a gain of 7.5.