Chapter 7, Solution 20.

(a)
$$\tau = \frac{L}{R} = \frac{1}{50} \longrightarrow R = 50L$$

$$v = -L \frac{di}{dt}$$

$$90e^{-50t} = -L(30)(-50)e^{-50t} \longrightarrow L = 60 \text{ mH}$$

$$R = 50L = 3 \Omega$$

(b)
$$\tau = \frac{L}{R} = \frac{1}{50} = 20 \text{ ms}$$

(c)
$$w = \frac{1}{2}Li^2(0) = \frac{1}{2}(0.06)(30)^2 = 27 J$$

The value of the energy remaining at 10 ms is given by:

$$w_{10} = 0.03(30e^{-0.5})^2 = 0.03(18.196)^2 = 9.933 \text{ J}.$$

So, the fraction of the energy dissipated in the first 10 ms is given by:

$$(27-9.933)/27 = 0.6321$$
 or **63.21%**.