

**Chapter 6, Problem 66.**

The current  $i(t)$  through a 20-mH inductor is equal, in magnitude, to the voltage across it for all values of time. If  $i(0) = 2$  A, find  $i(t)$ .