

**Chapter 6, Problem 23.**

Using Fig. 6.57, design a problem to help other students better understand how capacitors work together when connected in series and parallel.

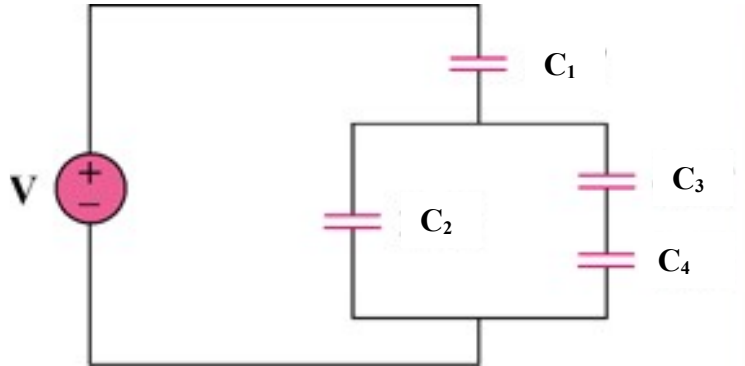


Figure 6.57  
For Prob. 6.23.