

Chapter 9, Problem 64.

Find \mathbf{Z}_T and \mathbf{I} in the circuit shown in Fig. 9.71.

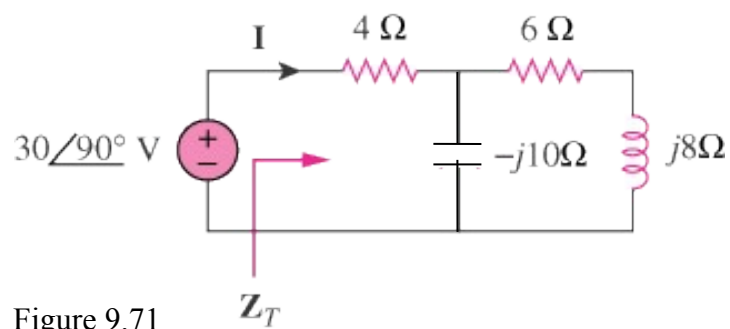


Figure 9.71
For Prob. 9.64.