

Chapter 5, Problem 13

Find v_o and i_o in the circuit of Fig. 5.52.

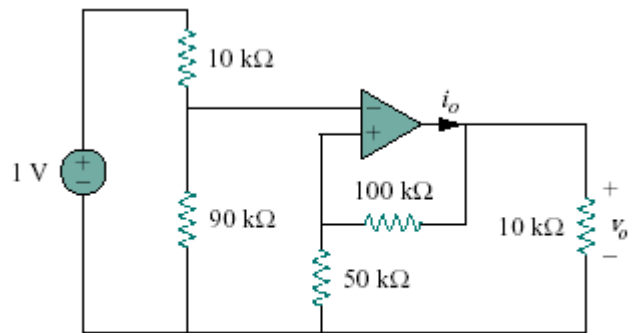


Figure 5.52
For Prob. 5.13.