

Chapter 10, Problem 5.

Find i_o in the circuit of Fig. 10.54.

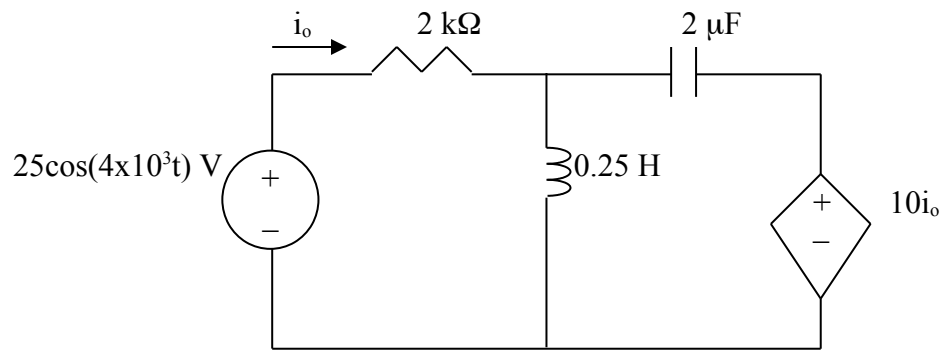


Figure 10.54
For Prob. 10.5.