

Chapter 10, Problem 32.

Determine V_o and I_o in the circuit of Fig. 10.80 using mesh analysis.

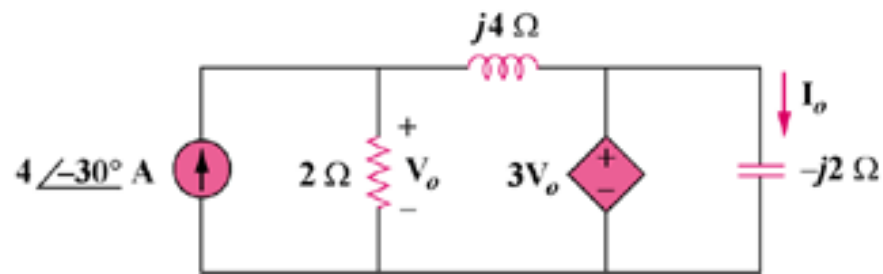


Figure 10.80
For Prob. 10.32.