

**Chapter 7, Problem 4.**

The switch in Fig. 7.84 moves instantaneously from A to B at  $t=0$ . Find  $v$  for  $t>0$ .

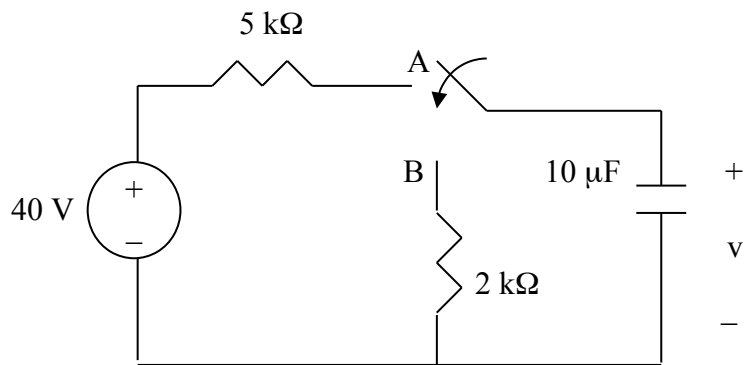


Figure 7.84  
For Prob. 7.4.