

Chapter 9, Problem 88.

A series audio circuit is shown in Fig. 9.88.

- (a) What is the impedance of the circuit?
- (b) If the frequency were halved, what would be the impedance of the circuit?

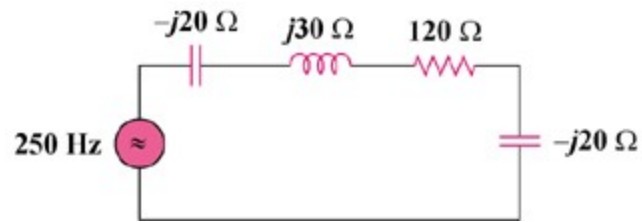


Figure 9.88
For Prob. 9.88.