

**Chapter 6, Problem 1.**

If the voltage across a 7.5-F capacitor is  $2te^{-3t}$  V, find the current and the power.