

Chapter 9, Problem 65.

Determine \mathbf{I} and \mathbf{Z}_T for the circuit in Fig. 9.72.

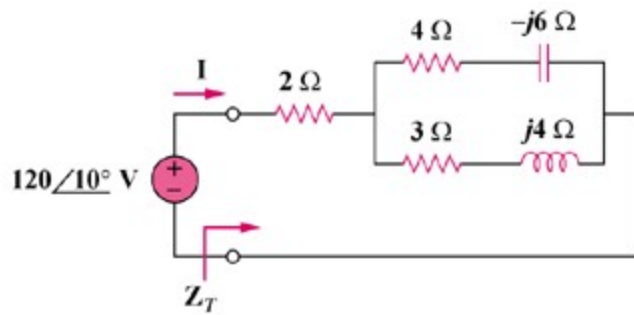


Figure 9.72
For Prob. 9.65.