

Chapter 10, Problem 11.

Using nodal analysis, find $i_o(t)$ in the circuit in Fig. 10.60.

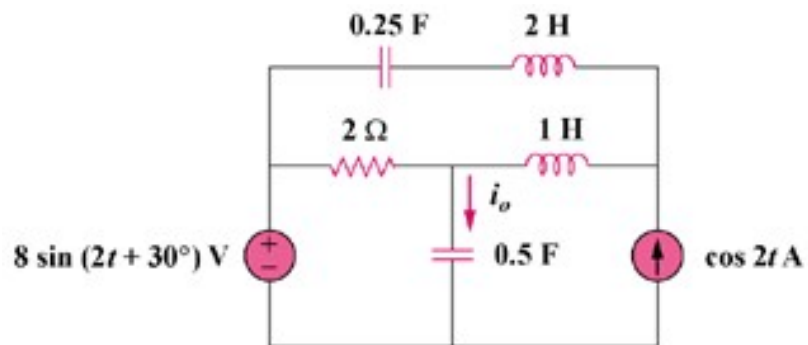


Figure 10.60
For Prob. 10.11.