

**Chapter 11, Problem 57.**

For the circuit in Fig. 11.76, find the average, reactive, and complex power delivered by the dependent voltage source.

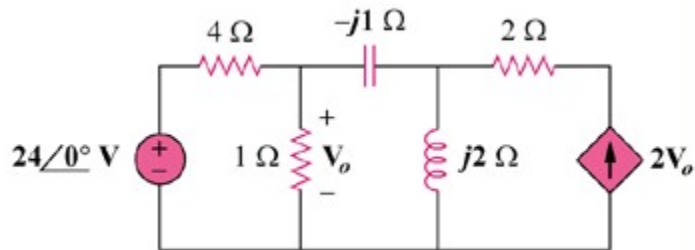


Figure 11.76  
For Prob. 11.57.