

**Chapter 10, Problem 66.**

At terminals  $a$ - $b$ , obtain Thevenin and Norton equivalent circuits for the network depicted in Fig. 10.109. Take  $\omega = 10$  rad/s.

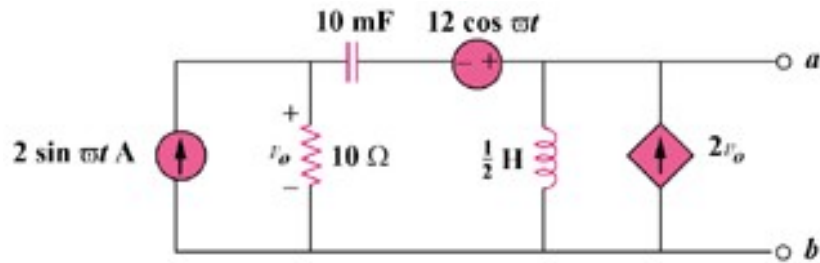


Figure 10.109  
For Prob. 10.66.