

**Chapter 11, Problem 20.**

The load resistance  $R_L$  in Fig. 11.51 is adjusted until it absorbs the maximum average power. Calculate the value of  $R_L$  and the maximum average power.

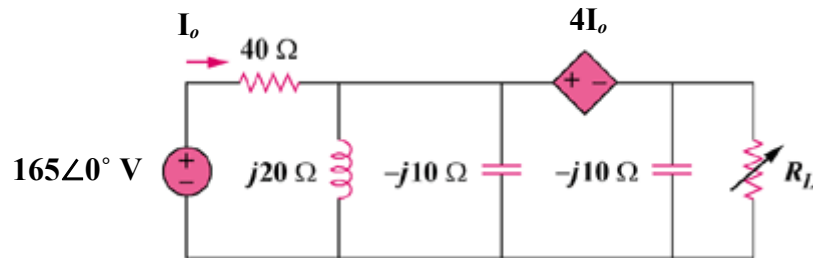


Figure 11.51  
For Prob. 11.20.