

Chapter 11, Problem 15.

In the circuit of Fig. 11.46, find the value of \mathbf{Z}_L that will absorb the maximum average power and the value of the maximum power.

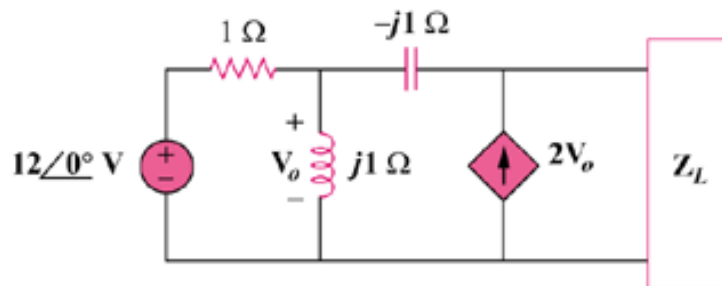


Figure 11.46
For Prob. 11.15.