

Chapter 11, Problem 5.

Assuming that $v_s = 8\cos(2t - 40^\circ)$ V in the circuit shown in Fig. 11.38, find the average power delivered to each of the passive elements.

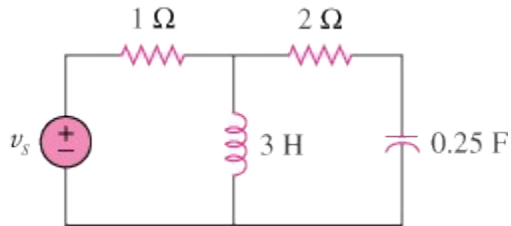


Figure 11.38
For Prob. 11.5.