

### Chapter 11, Solution 20.

The load resistance  $R_L$  in Fig. 11.51 is adjusted until it absorbs the maximum average power. Calculate the value of  $R_L$  and the maximum average power.


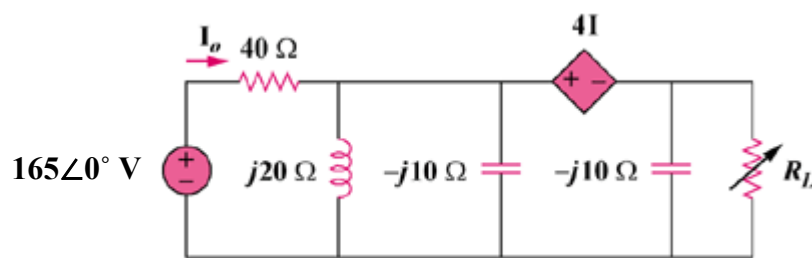


Figure 11.51  
For Prob. 11.20.
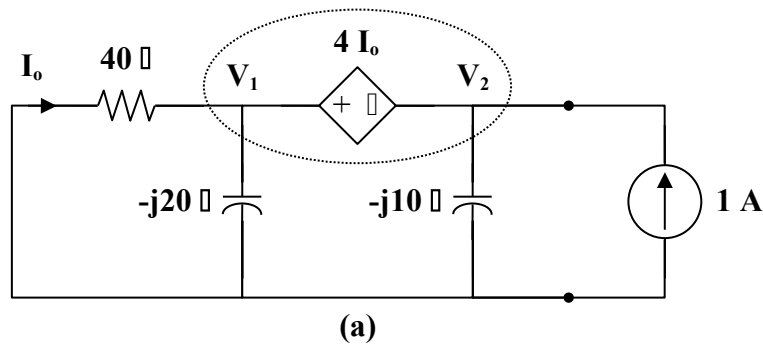
### Solution

Combine  $j20 \parallel$  and  $-j10 \parallel$  to get  $j20 \parallel -j10 = -j20$ .

To find  $\mathbf{Z}_{Th}$ , insert a 1-A current source at the terminals of  $R_L$ , as shown in Fig. (a).



At the supernode,

$$1 = \frac{V_1}{40} + \frac{V_1}{-j20} + \frac{V_2}{-j10}$$

$$40 = (1 + j2)V_1 + j4V_2 \quad (1)$$

Also,  $V_1 = V_2 + 4I_o$ , where  $I_o = \frac{-V_1}{40}$

$$1.1V_1 = V_2 \longrightarrow V_1 = \frac{V_2}{1.1} \quad (2)$$


Substituting (2) into (1),

$$40 = (1 + j2)\left(\frac{V_2}{1.1}\right) + j4V_2$$

$$\mathbf{V}_2 = \frac{44}{1 + j6.4}$$

$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_2}{1} = 1.05 - j6.71 \, \Omega$$

$$\mathbf{R}_L = |\mathbf{Z}_{Th}| = \mathbf{6.792 \, \Omega}$$

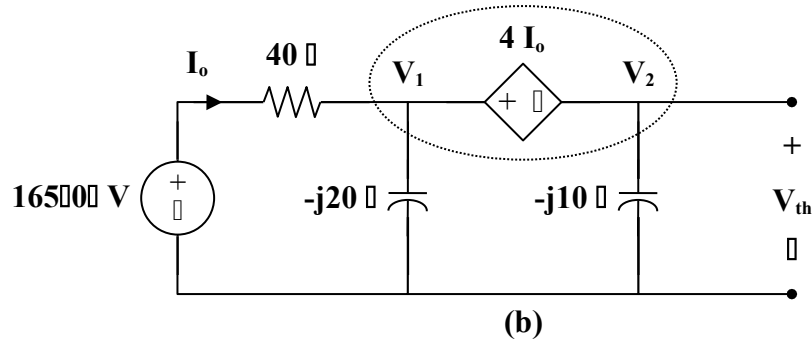

To find  $\mathbf{V}_{Th}$ , consider the circuit in Fig. (b).

At the supernode,

$$\begin{aligned} \frac{165 - \mathbf{V}_1}{40} &= \frac{\mathbf{V}_1}{-j20} + \frac{\mathbf{V}_2}{-j10} \\ 165 &= (1 + j2)\mathbf{V}_1 + j4\mathbf{V}_2 \end{aligned} \quad (3)$$

Also,

$$\begin{aligned} \mathbf{V}_1 &= \mathbf{V}_2 + 4\mathbf{I}_o, \text{ where } \mathbf{I}_o = \frac{165 - \mathbf{V}_1}{40} \\ \mathbf{V}_1 &= \frac{\mathbf{V}_2 + 16.5}{1.1} \end{aligned} \quad (4)$$

Substituting (4) into (3),

$$150 - j30 = (0.9091 + j5.818)\mathbf{V}_2$$

$$\mathbf{V}_{Th} = \mathbf{V}_2 = \frac{150 - j30}{0.9091 + j5.818} = \frac{152.97 \angle -11.31^\circ}{5.889 \angle 81.12^\circ} = 25.98 \angle -92.43^\circ$$

$$\mathbf{P}_{max} = \left| \frac{25.98}{1.05 - j6.71 + 6.792} \right|^2 \frac{6.792}{2} = \mathbf{21.51 \, W}$$