

### Chapter 10, Solution 43.

Using the superposition principle, find  $i_x$  in the circuit of Fig. 10.88.

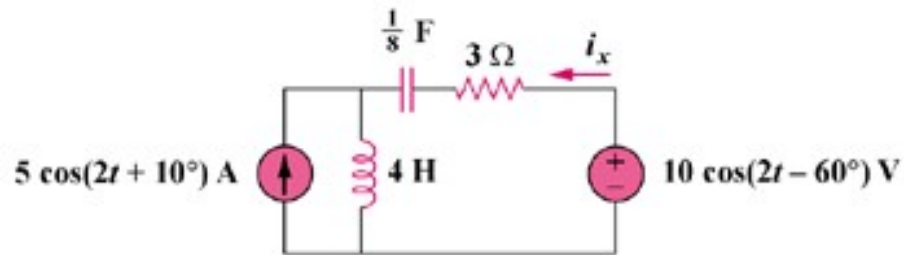


Figure 10.88  
For Prob. 10.43.

### Solution

Let  $\mathbf{I}_x = \mathbf{I}_1 + \mathbf{I}_2$ , where  $\mathbf{I}_1$  is due to the voltage source and  $\mathbf{I}_2$  is due to the current source.

$$\omega = 2$$


$$5 \cos(2t + 10^\circ) \longrightarrow 5 \angle 10^\circ$$

$$10 \cos(2t - 60^\circ) \longrightarrow 10 \angle -60^\circ$$


$$4 \text{ H} \longrightarrow j\omega L = j8$$

$$\frac{1}{8} \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(2)(1/8)} = -j4$$

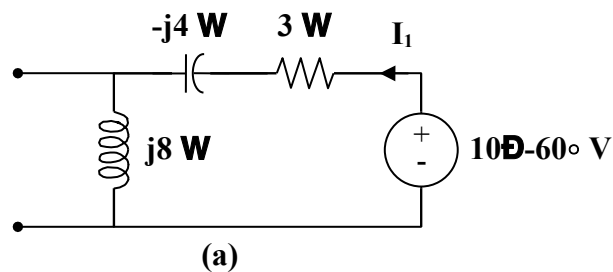For  $\mathbf{I}_1$ , consider the circuit in Fig. (a).


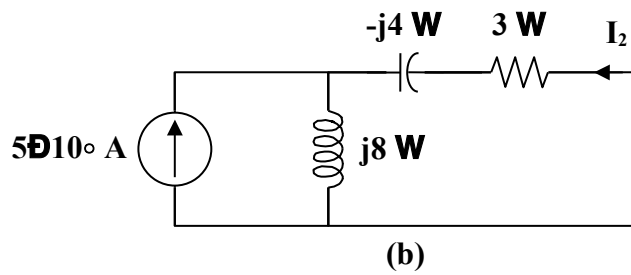
$$\mathbf{I}_1 = \frac{10 \angle -60^\circ}{3 + j8 - j4} = \frac{10 \angle -60^\circ}{3 + j4}$$



For  $\mathbf{I}_2$ , consider the circuit in Fig. (b).

$$\mathbf{I}_2 = \frac{-j8}{3 + j8 - j4} (5\angle 10^\circ) = \frac{-j40\angle 10^\circ}{3 + j4}$$

$$\mathbf{I}_x = \mathbf{I}_1 + \mathbf{I}_2 = \frac{1}{3 + j4} (10\angle -60^\circ - j40\angle 10^\circ)$$

$$\mathbf{I}_x = \frac{49.51\angle -76.04^\circ}{5\angle 53.13^\circ} = 9.902\angle -129.17^\circ$$

Therefore,  $i_x = 9.902 \cos(2t - 129.17^\circ) \text{ A}$