

Chapter 9, Problem 54.

In the circuit of Fig. 9.61, find V_s if $I_o = 2\angle 0^\circ$ A.

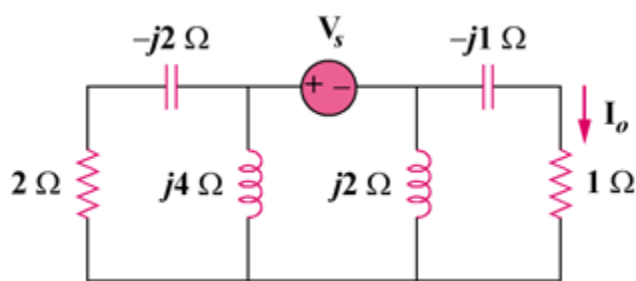


Figure 9.61
For Prob. 9.54.