

Chapter 11, Problem 1.

If $v(t) = 160 \cos 50t$ V and $i(t) = -33 \sin (50t - 30^\circ)$ A, calculate the instantaneous power and the average power.