

**Chapter 9, Problem 37.**

Determine the admittance  $\mathbf{Y}$  for the circuit in Fig. 9.44.

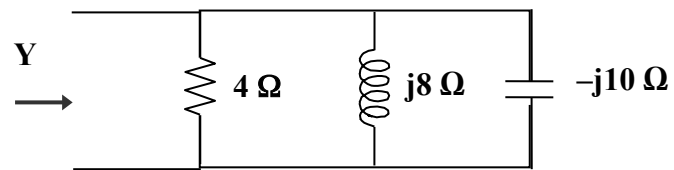


Figure 9.44  
For Prob. 9.37.