

Chapter 6, Problem 69.

An op amp integrator with $R = 4\text{ M}\Omega$ and $C = 1\text{ }\mu\text{F}$ has the input waveform shown in Fig. 6.88. Plot the output waveform.

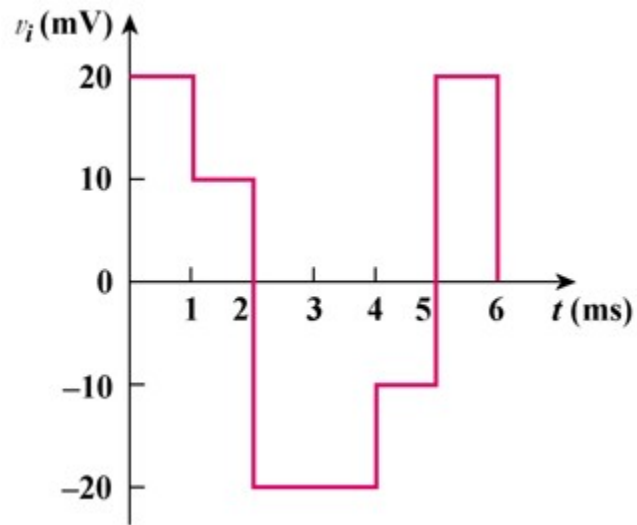


Figure 6.88
For Prob. 6.69.