

Chapter 10, Problem 31.

Use mesh analysis to determine current \mathbf{I}_o in the circuit of Fig. 10.79 below.

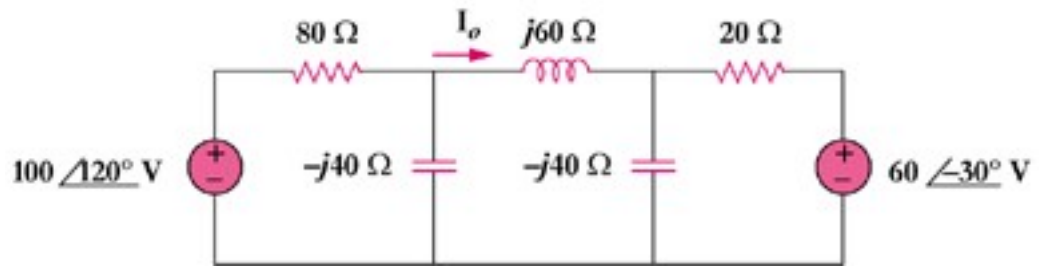


Figure 10.79
For Prob. 10.31.