

**Chapter 6, Problem 77.**

The output  $v_o$  of the op amp circuit of Fig. 6.92(a) is shown in Fig. 6.92(b). Let  $R_i = R_f = 1\text{ M}\Omega$  and  $C = 1\text{ }\mu\text{F}$ . Determine the input voltage waveform and sketch it.

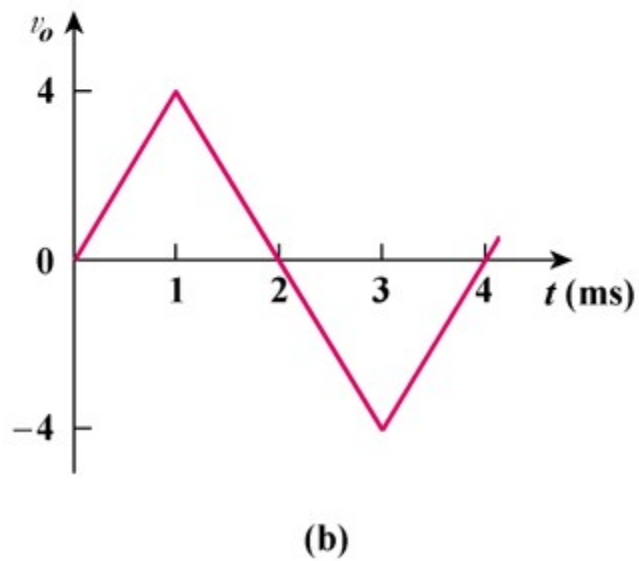
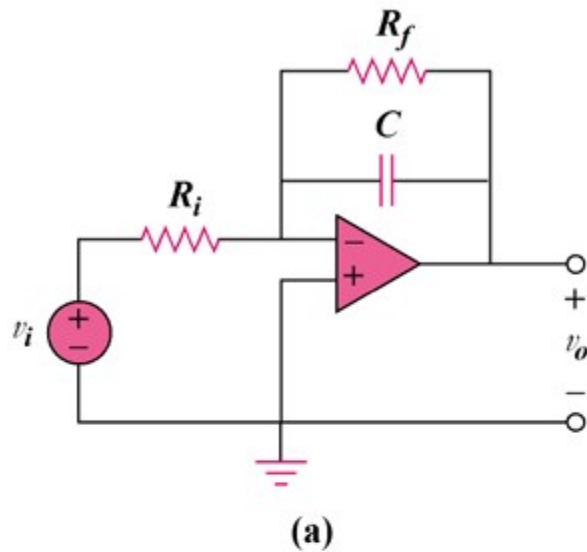


Figure 6.92  
For Prob. 6.77.