

**Chapter 5, Problem 63.**

Determine the gain  $v_o/v_i$  of the circuit in Fig. 5.90.

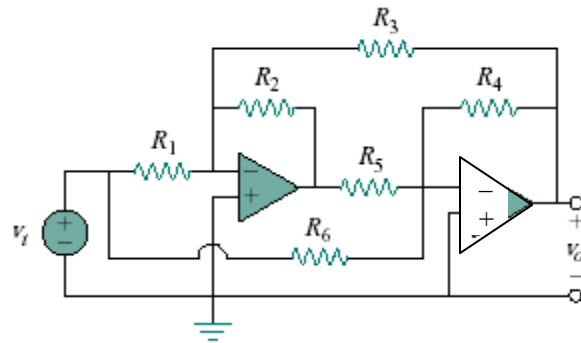


Figure 5.90  
For Prob. 5.63.