

Chapter 9, Problem 55.

Find \mathbf{Z} in the network of Fig. 9.62, given that $\mathbf{V}_o = 4\angle 0^\circ \text{ V}$

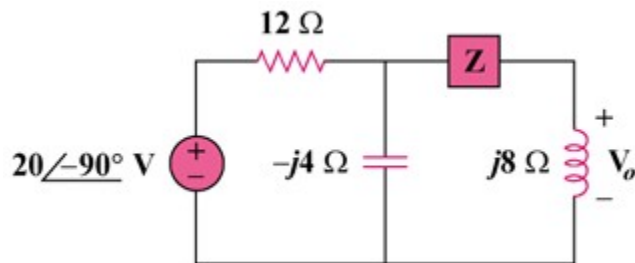


Figure 9.62
For Prob. 9.55.