

**Chapter 7, Problem 56.**

For the network shown in Fig. 7.122, find  $v(t)$  for  $t > 0$ .

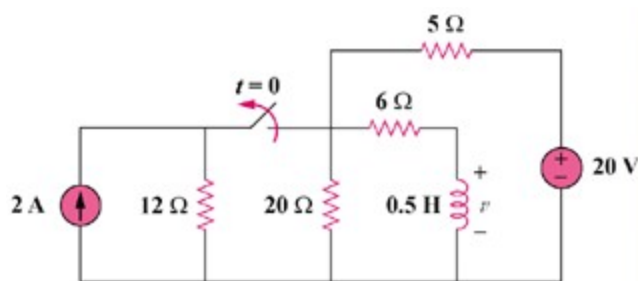


Figure 7.122  
For Prob. 7.56.