

**Chapter 5, Solution 89.**

A **summer** with  $v_o = -v_1 - (5/3)v_2$  where  $v_2 = 6\text{-V battery}$  and an **inverting amplifier** with  $v_1 = -12v_s$ .